

## DN95

# 2.8A high current LED driving using ZXLD1320 with external power switch

Ray Liu, Applications engineer, Diodes Incorporated

### Introduction

In the past decade, solid state lighting devices have gained popularity. High brightness LEDs are finding their way into a wide range of applications. High power capacity multi-chip LED devices now often require higher LED driving current than previously.

The ZXLD1320 is a buck LED driver IC with built in 2A bipolar power switch which is capable of driving high power LED with constant LED current up to 1.5A. Higher LED driving current can be achieved with additional external power switch.

The following are design examples of two 2.8A constant current LED driver circuits which are capable to drive multi-chip LED devices likes the Cree XLamp MC-E or the Seoul Semiconductor Z-Power P7 .

### 2.8A LED driver with external MOSFET switch

Figure 1 and Table 1 show the schematic and bill of materials of 2.8A step down LED driver circuit for input voltage ranged from 4V up to 18V.

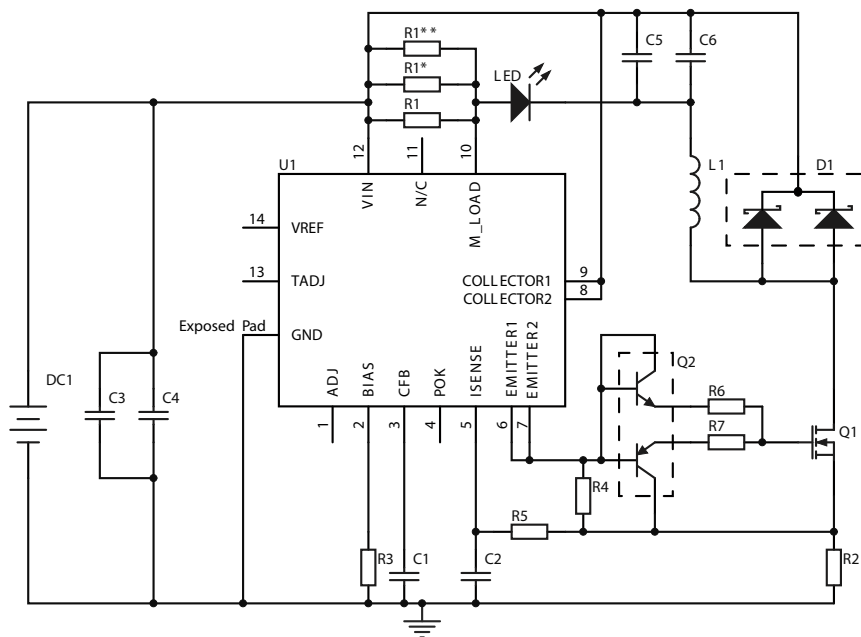


Figure 1 - Schematic

# DN95

Ref No.	Value	Part No.	Manufacturer	Website
U1	LED Driver	ZXLD1320	Diodes Zetex	<a href="http://www.diodes.com">www.diodes.com</a> <a href="http://www.zetex.com">www.zetex.com</a>
Q1	MOSFET	ZXMN3A04KTC	Diodes Zetex	<a href="http://www.diodes.com">www.diodes.com</a> <a href="http://www.zetex.com">www.zetex.com</a>
Q2	Gate Driver BJT Pairs	ZXTC2045	Diodes Zetex	<a href="http://www.diodes.com">www.diodes.com</a> <a href="http://www.zetex.com">www.zetex.com</a>
D1	Super Barrier Rectifier	SBR1045CT	Diodes Zetex	<a href="http://www.diodes.com">www.diodes.com</a> <a href="http://www.zetex.com">www.zetex.com</a>
L1	10uH 4.1A	74477110 NPIS24H100MTRF MSS1246-103ML	Würth Elektronik NIC Coilcraft	<a href="http://www.we-online.com">www.we-online.com</a> <a href="http://www.niccomp.com">www.niccomp.com</a> <a href="http://www.coilcraft.com">www.coilcraft.com</a>
C1	10nF 25V X7R SMD 0603	NMC0603X7R103K25TRPF GRM188R71E103KA01	NIC Murata	<a href="http://www.niccomp.com">www.niccomp.com</a> <a href="http://www.murata.com">www.murata.com</a>
C2	47nF 25V X7R SMD 0603	NMC0603X7R473K25TRPF GRM188R71E473KA01	NIC Murata	<a href="http://www.niccomp.com">www.niccomp.com</a> <a href="http://www.murata.com">www.murata.com</a>
C3 C4 C5 C6	4.7uF 50V X7R SMD 1206	GRM31CR71H475KA12	Murata	<a href="http://www.murata.com">www.murata.com</a>
R1 R1*	100mΩ	NCST12FR100FTRF	NIC	<a href="http://www.niccomp.com">www.niccomp.com</a>
R1**	120mΩ	NCST12FR100FTRF	NIC	<a href="http://www.niccomp.com">www.niccomp.com</a>
R2	15mΩ	SMD 1206	generic	
R3 R7	0Ω	SMD 0805 / 0603	generic	
R4	1.2KΩ	SMD 0805 / 0603	generic	
R5	33Ω	SMD 0805 / 0603	generic	
R6	5.6Ω	SMD 0805 / 0603	generic	

Table 1 - Bill of materials

## Circuit description

In this design, the ZXLD1320 is used as current feedback controller to control the MOSFET power switch through a ZXTC2045 gate drive transistor pair.



The output switch of ZXLD1320 is configured as an emitter-follower which becomes part of the gate drive circuitry. Q2 is a complementary BJT pair with the NPN transistor connected as a blocking diode.

During the on-state, the NPN transistor is bypassed and the driving current from ZXLD1320 Emitter pin charges up the gate of the MOSFET, causing the MOSFET to turn on. During the off-state, the PNP transistor turns on due to passive pull down of R4. This acts as an active pull down to discharge the gate of the MOSFET, causing the MOSFET to turn off.

The super barrier rectifier SBR1045CT is selected as the free wheeling rectifier D1 due to its ultra-low forward voltage characteristic and its much better reverse leakage current. This helps to improve the overall system conversion efficiency.

A voltage spike is generated by high switching current and stray inductance of PCB's copper track. This would be high compared to the low ISENSE voltage threshold of ZXLD1320 which is below 55mV. An RC filter formed by C2 and R5 is used to prevent false triggering of ISENSE pin. C2 should be placed as close as possible to the ISENSE pin and the exposed GND pad of the IC.

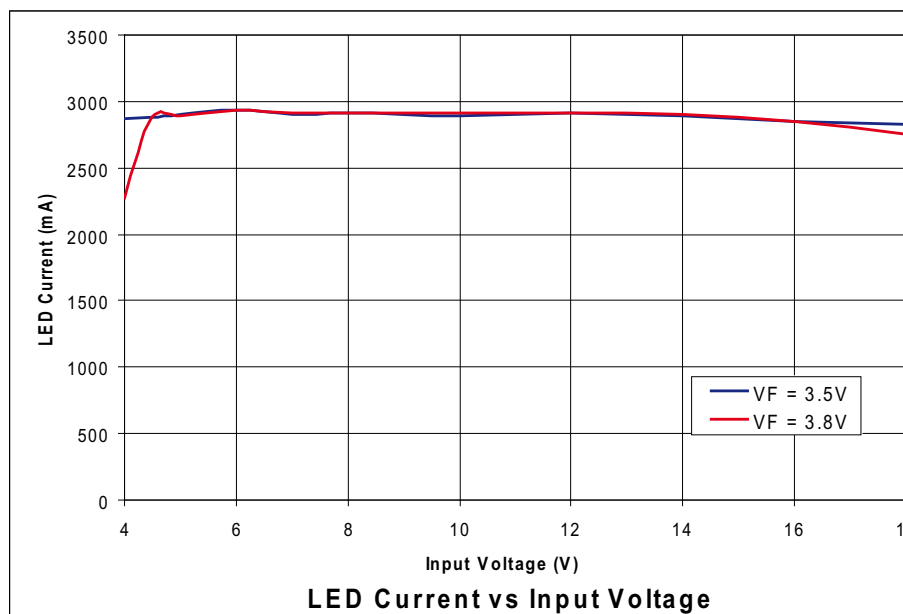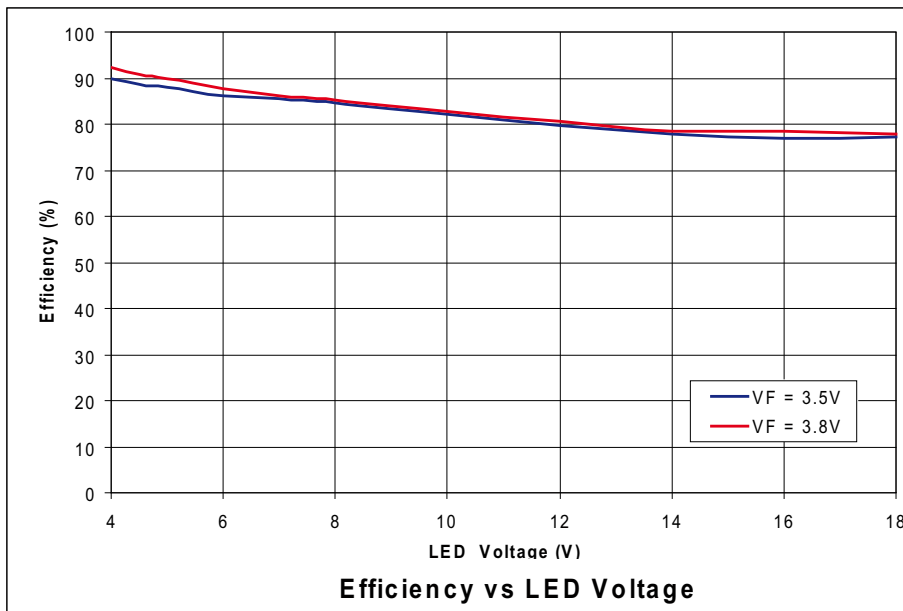Typical performance (MOSFET power switch)



A high performance BJT could also be used as power switch with good performance at lower working voltage range

# DN95

## 2.8A LED driver with external BJT switch

Figure 2 and Table 2 show the schematic and bill of material of 2.8A step down LED driver for input voltage ranged from 4.5V up to 7.5V.

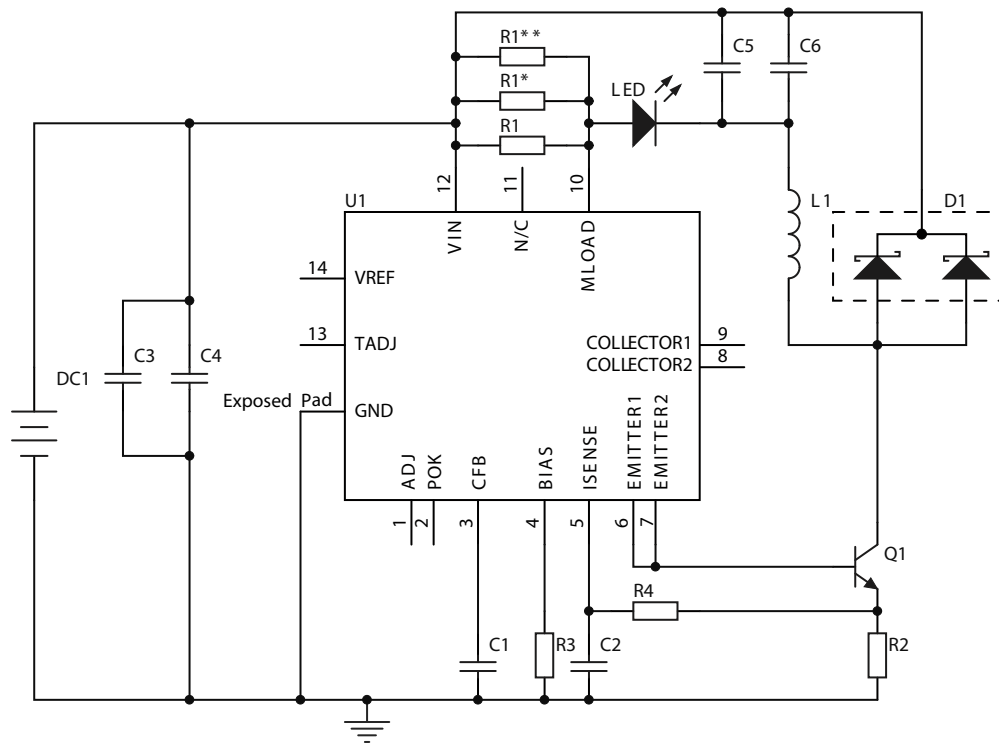


Figure 2 - Schematic

Ref No.	Value	Part No.	Manufacturer	Note
U1	LED Driver	ZXLD1320	Diodes Zetex	<a href="http://www.diodes.com">www.diodes.com</a> <a href="http://www.zetex.com">www.zetex.com</a>
Q1	Super Transistor	ZXTN25012EZ	Diodes Zetex	<a href="http://www.diodes.com">www.diodes.com</a> <a href="http://www.zetex.com">www.zetex.com</a>
D1	Super Barrier Rectifier	SBR1045CT	Diodes Zetex	<a href="http://www.diodes.com">www.diodes.com</a> <a href="http://www.zetex.com">www.zetex.com</a>
L1	10uH 4.1A	74477110	Würth Elektronik	<a href="http://www.we-online.com">www.we-online.com</a>
C1	10nF 25V X7R	SMD 0805 / 0603		
C2	47nF 25V X7R	SMD 0805 / 0603		
C3 C4 C5 C6	4.7uF 25V X7R	SMD 1206		
R1 R1*	100mΩ	SMD 1206		
R1**	120mΩ	SMD 1206		
R2	15mΩ	SMD 1206		
R3	220Ω	SMD 0805 / 0603		
R4	33Ω	SMD 0805 / 0603		

Table 2 - Bill of materials

## Circuit description



This circuit is similar to the MOSFET switch circuit. The gate driver transistor and MOSFET is replaced by single ZXTN25012EZ bipolar transistor. In this case, the COLLECTOR pins of ZXLD1320 are not connected to VCC. i.e. the ZXTN25012EZ is driven by the ZXLD1320's internal driver through the BE junction of internal bipolar switch.

R3 is set to 220 Ohm to supply 25mA of drive current. Adequate base driving current is essential to prevent excess minority charge accumulating in the base region of the ZXTN25012EZ. This causes the transistor to go into deep saturation which stores charge. The removal of this excess charge will actually increase the rise time during turn off state.

A BJT exhibits higher rise/fall time compared to MOSFET. The switching losses become significant as switching voltage and frequency increase. i.e. Input voltages of greater than 9V are not recommended for this design.

# DN95
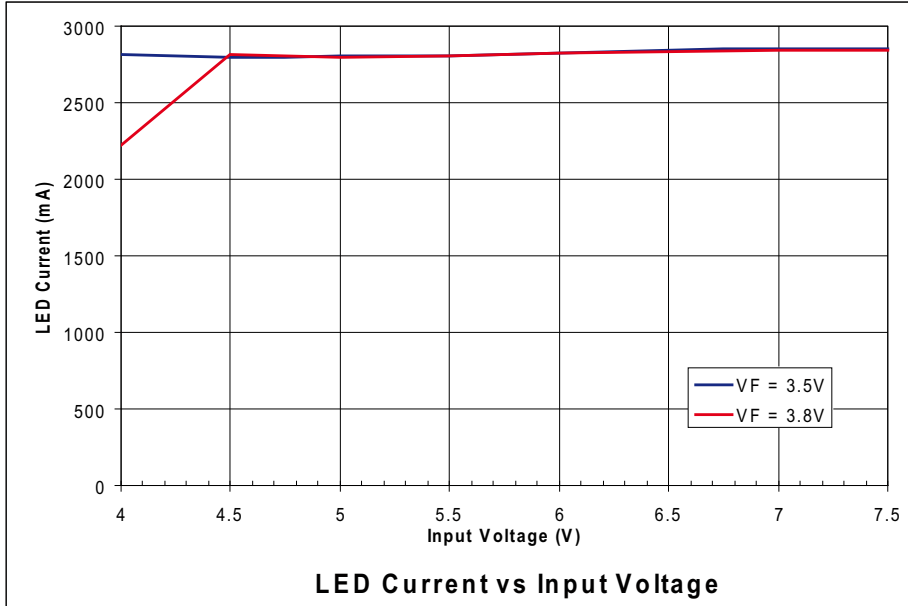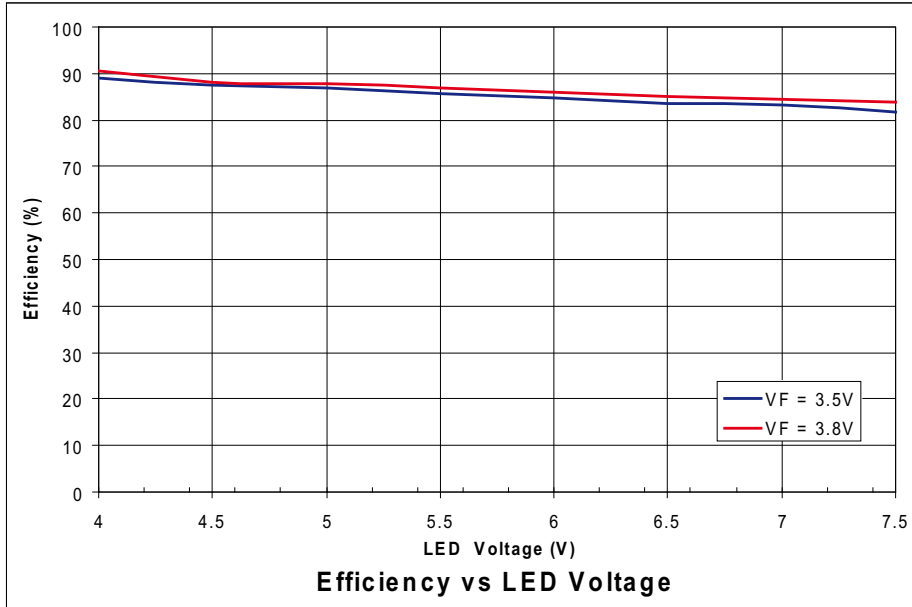
## Typical performance graphs (BJT Power Switch)



## Conclusion

Bipolar and Mosfet power switches could be connected to ZXLD1320 to produce a high current buck type LED drivers with scalable output current capability at an efficiency of around 85%. If power supply voltage is below 8V, bipolar power switch is recommended with less component count. For application with higher input voltage, efficiency of bipolar switch drop quickly as input voltage increase. Mosfet switch shows better efficiency performance over the whole input voltage range.

# DN95



# DN95

## Definitions

### Product change

Diodes Incorporated the right to alter, without notice, specifications, design, price or conditions of supply of any product or service. Customers are solely responsible for obtaining the latest relevant information before placing orders.

### Applications disclaimer

The circuits in this design/application note are offered as design ideas. It is the responsibility of the user to ensure that the circuit is fit for the user's application and meets with the user's requirements. No representation or warranty is given and no liability whatsoever is assumed by Diodes Inc. with respect to the accuracy or use of such information, or infringement of patents or other intellectual property rights arising from such use or otherwise. Diodes Inc. does not assume any legal responsibility or will not be held legally liable (whether in contract, tort (including negligence), breach of statutory duty, restriction or otherwise) for any damages, loss of profit, business, contract, opportunity or consequential loss in the use of these circuit applications, under any circumstances.

### Life support

Diodes Zetex products are specifically not authorized for use as critical components in life support devices or systems without the express written approval of the Chief Executive Officer of Diodes Incorporated. As used herein:

A. Life support devices or systems are devices or systems which:

1. are intended to implant into the body

or

2. support or sustain life and whose failure to perform when properly used in accordance with instructions for use provided in the labelling can be reasonably expected to result in significant injury to the user.

B. A critical component is any component in a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or to affect its safety or effectiveness.

### Reproduction

The product specifications contained in this publication are issued to provide outline information only which (unless agreed by the company in writing) may not be used, applied or reproduced for any purpose or form part of any order or contract or be regarded as a representation relating to the products or services concerned.

### Terms and Conditions

All products are sold subjects to Diodes Inc. terms and conditions of sale, and this disclaimer (save in the event of a conflict between the two when the terms of the contract shall prevail) according to region, supplied at the time of order acknowledgement.

For the latest information on technology, delivery terms and conditions and prices, please contact your nearest Diodes' sales office .

### Quality of product

Diodes Zetex Semiconductors Limited is an ISO 9001 and TS16949 certified semiconductor manufacturer.

To ensure quality of service and products we strongly advise the purchase of parts directly from Diodes Inc. or one of our regionally authorized distributors. For a complete listing of authorized distributors please visit: [www.diodes.com](http://www.diodes.com)

Diodes Zetex does not warrant or accept any liability whatsoever in respect of any parts purchased through unauthorized sales channels.

### ESD (Electrostatic discharge)

Semiconductor devices are susceptible to damage by ESD. Suitable precautions should be taken when handling and transporting devices. The possible damage to devices depends on the circumstances of the handling and transporting, and the nature of the device. The extent of damage can vary from immediate functional or parametric malfunction to degradation of function or performance in use over time. Devices suspected of being affected should be replaced.

### Green compliance

Diodes Zetex Semiconductors is committed to environmental excellence in all aspects of its operations which includes meeting or exceeding regulatory requirements with respect to the use of hazardous substances. Numerous successful programs have been implemented to reduce the use of hazardous substances and/or emissions.

All Diodes Zetex components are compliant with the RoHS directive, and through this it is supporting its customers in their compliance with WEEE and ELV directives.

### Product status key:

"Preview"	Future device intended for production at some point. Samples may be available
"Active"	Product status recommended for new designs
"Last time buy (LTB)"	Device will be discontinued and last time buy period and delivery is in effect
"Not recommended for new designs"	Device is still in production to support existing designs and production
"Obsolete"	Production has been discontinued

### Datasheet status key:

"Draft version"	This term denotes a very early datasheet version and contains highly provisional information, which may change in any manner without notice.
"Provisional version"	This term denotes a pre-release datasheet. It provides a clear indication of anticipated performance. However, changes to the test conditions and specifications may occur, at any time and without notice.
"Issue"	This term denotes an issued datasheet containing finalized specifications. However, changes to specifications may occur, at any time and without notice.

## Sales offices

The Americas	Europe	Taiwan	Shanghai	Shenzhen	Korea
3050 E. Hillcrest Drive Westlake Village, CA 91362-3154 Tel: (+1) 805 446 4800 Fax: (+1) 805 446 4850	Kustermann-Park Balanstraße 59, D-81541 München Germany Tel: (+49) 894 549 490 Fax: (+49) 894 549 4949	7F, No. 50, Min Chuan Road Hsin-Tien Taipei, Taiwan Tel: (+886) 289 146 000 Fax: (+886) 289 146 639	Rm. 606, No.1158 Changning Road Shanghai, China Tel: (+86) 215 241 4882 Fax (+86) 215 241 4891	ANLIAN Plaza, #4018 Jintian Road Futian CBD, Shenzhen, China Tel: (+86) 755 882 849 88 Fax: (+86) 755 882 849 99	6 Floor, Changhwa B/D, 1005-5 Yeongtong-dong, Yeongtong-gu, Suwon-si, Gyeonggi-do, Korea 443-813 Tel: (+82) 312 731 884 Fax: (+82) 312 731 885

# DN95