
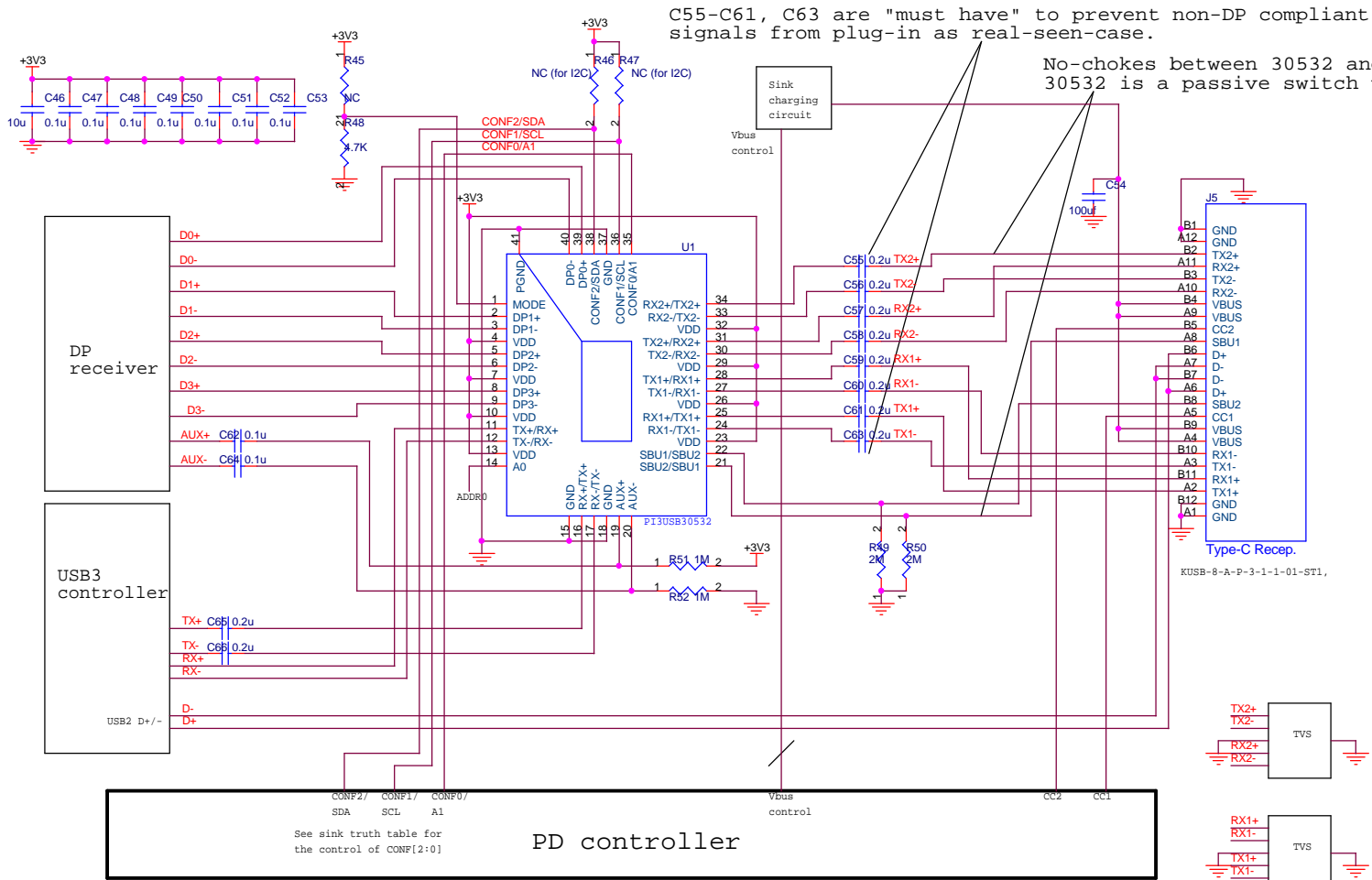


C55-C61, C63 are "must have" to prevent non-DP compliant 3.3V signals from plug-in as real-seen-case.

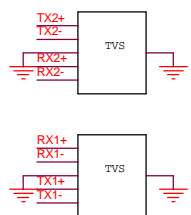No-chokes between 30532 and type-C connector, because 30532 is a passive switch without EMI issue.



PI3USB30532 reference schematic for sink application



Contact Diodes local sales for TVS