

# AL8862Q Input Filter Design for CISPR 25 Compliance

Touheed Khan and Naveed Chowdhury, Automotive Applications Engineers, Diodes Incorporated

Diodes Incorporated Buck LED drivers, AL8860Q, AL8861Q and AL8862Q, provide low-cost and robust solutions for driving high-current LEDs in interior and exterior automotive lighting applications. The flexibility, owing to their hysteretic control scheme and adjustable frequency, enables designers to minimize overall system size and cost.

This design example uses the standard AL8862QEV1 evaluation board as shown in Figure 1. This board is designed to demonstrate and evaluate the AL8862Q in an SO-8EP package for applications such as headlights and taillights. This board was not optimised to pass CISPR 25 automotive EMC standard. This application note discusses the input filter(s) that need to be implemented in order to ensure that the design passes CISPR 25 Class 4 conducted emissions while optimizing board space and system efficiency.

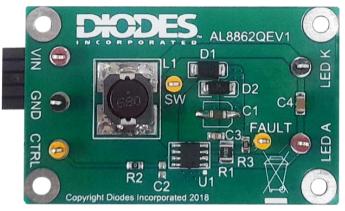


Figure 1: AL8862QEV1

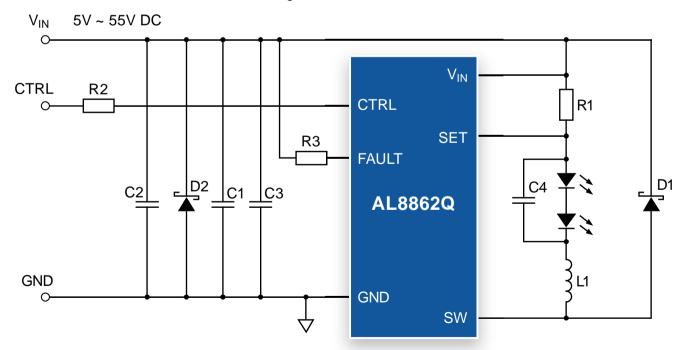


Figure 2: AL8862QEV1 Schematic



# Procedure for Input Filter Design:

For details on the LED converter implementation, please refer to the datasheet of <u>AL8862Q</u>. The filter design is dependent on the selection of values for  $C_{f1}$  and  $L_f$ .  $C_{f2}$  is optional but may be necessary to provide damping to avoid instability in the filter.

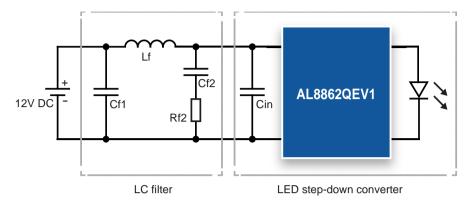


Figure 3: Input LC filter cascaded with an LED driver based on AL8862Q DC-DC converter.

#### Steps in Filter Design:

Step 1. Select  $C_{in}$  according to AL8862Q datasheet.

Step 2. Measure the noise across the CISPR 25 frequency range.

Step 3. Determine filter attenuation based on the noise and target CISPR 25 limits.

Step 4. Select  $L_f$  according to methodology below.

Step 5. Calculate  $C_{f1}$  according to methodology below.

Step 6: Selection of  $C_{f2}$  and  $R_{f2}$ . It is also important to consider the damping of the filter. High Q filters can be prone to instability with switching loads.

Note: this filter is not effective at reducing common mode (CM) noise on input lines if CM noise exists.

#### Input Capacitor Selection (C<sub>in</sub>):

The input supply to the AL8862Q must be decoupled to ground with a low ESR ceramic capacitor (X7R recommended) immediately next to the VIN pin. The input ripple voltage amplitude is directly proportional to the LED load current. To determine a suitable size for the input capacitor, the following equation can be used.

$$C_{in(min)} = \frac{D \times (1-D) \times I_{LED}}{V_{pk-pk(ripple)} \times f_{SW}}$$

Where:

 $C_{in(min)}$  (F) is the recommended minimum input capacitance for the DC-DC LED converter.

 $f_{sw}$  (Hz) is the switching frequency of the DC-DC LED driver.

 $I_{LED}$  (A) is the average LED output current.

 $V_{pk-pk(ripple)}$  (V) is the peak-to-peak ripple voltage at the input. With 9.4µF input capacitance and 0.54 duty cycle it is typically 150mV.

D is the duty cycle of the step-down DC-DC LED converter. The duty cycle can be approximated using the Equation below with an estimated diode forward voltage ( $V_f = 0.5V$ ) and the LED driver internal MOSFET on-resistance ( $R_{DS(on)} = 0.4 \Omega$ ).

$$D = \frac{V_{out} + R_{DS(on)}I_{LED}}{V_{in} - V_F + R_{DS(on)}I_{LED}}$$

An input capacitance of  $9.4\mu$ F (2 x  $4.7\mu$ F) is utilised in the AL8862QEV1.



#### EMI Noise Estimation for Required Attenuation:

#### Using the Spectrum Analyser and Line Impedance Stabilization Network (LISN)

The conducted emissions can directly be measured in  $dB\mu V$  using a spectrum analyser and LISN. A LISN is an industrial instrument that creates an 'artificial network' and is intended to be installed between the EUT's power source and input.

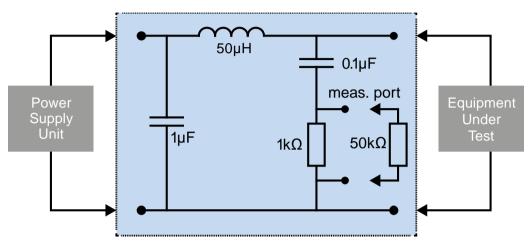


Figure 4: Internal circuit diagram of Las per the CISPR 25 automotive standard

#### **Component Selection:**

Example operating conditions are given in table 1:

| PARAMETER        | COMMENTS  | SPECIFICATION            |
|------------------|---|--------------------------|
| V <sub>in</sub>  | Automotive batteries' nominal operating voltage                         | 13.5V DC                 |
| V <sub>out</sub> | Total voltage across the LED chain anode to cathode (2x LEDs in series) | 7.15V DC                 |
| I <sub>LED</sub> | Average output current to the LEDs                                      | 1A                       |
| C <sub>in</sub>  | Input capacitance of the LED Driver                                     | 9.5μF<br>(2×4.7μF+0.1μF) |
| f <sub>sw</sub>  | Switching frequency of the AL8862Q under nominal operating conditions   | 175kHz                   |

Table 1: Example Operating Conditions



### CISPR 25 Sweep to Get Values for Required Attenuation.

The magnitude of the attenuation level has been measured by using the spectrum analyser and LISN circuit. The measured EMI are shown in the plot obtained from the spectrum analyser below:

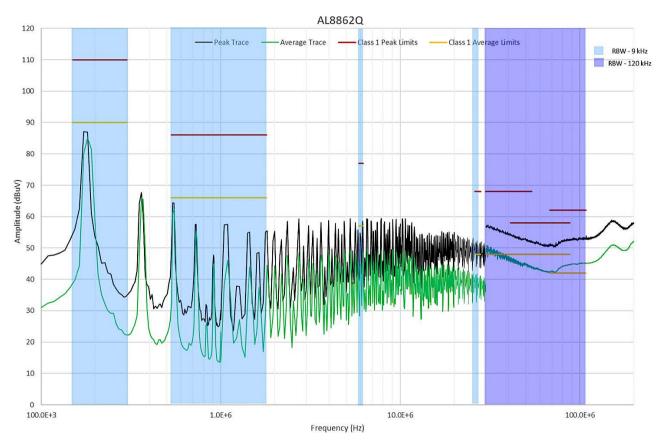


Figure 5: Plot obtained from spectrum analyser

The EMI peak, which occurs at the fundamental frequency is 88 dBµV. The AL8862Q is not complaint to any CISPR 25 class.

# Determine Filter Attenuation Based on the Noise and Target CISPR 25 Limits.

The fundamental frequency of the conducted noise is at the switching frequency of the LED driver. While higherorder harmonics will appear, the EMI at the fundamental (assuming within a CISPR 25 band) typically requires attenuation with additional input filtering to meet requirements. The LC filter is a single stage differential-mode filter with attenuation slope of -40 dB/decade (i.e., one inductor and one capacitor). This low component count makes this filter highly cost effective and efficient.

The safety Margin (dBµV) is chosen for the required attenuation and can be set to 20dB in a conservative case.

The largest peak in the sweep occurs at approximately 175kHz and is at 88dBµV, so we need to target this frequency and therefore our attenuation calculation is going to be based on this value.

The target filter attenuation required to meet CISPR 25 class 4, 80dBµV at this frequency, with a 20dBµV safety margin is calculated using equation:

 $Attenuation(dB\mu V) = Amplitude(dB\mu V) - CISPR LIMIT(dB\mu V) + SafetyMargin(dB\mu V)$ 

 $Attenuation(dB\mu V) = 88 - (80) + 20 = 28 (dB\mu V)$ 



# Selection of Filter Inductor $(L_f)$

For low to medium power LED applications, a suitable range for inductor values is from  $0.68\mu$ H to  $22\mu$ H. The filter inductor value is inversely proportional to the filter capacitor value i.e., for high rating of inductor, filter capacitor will be a low value and vice versa. The selected value of inductor is  $22\mu$ H to reduce capacitance value and current ripple.

### Selection of Filter Capacitor ( $C_{f1}$ )

The capacitor value is estimated using equation:

$$C_{f1} = \frac{1}{L_f (2\pi f_r)^2 - 1}$$

Where  $f_r$  is  $\frac{f_{SW}}{10}$ .

In this case we get:

$$C_{f1} = \frac{1}{22 \times 10^{-6} (2 \times 3.14 \times 17.5 \times 10^3)^2 - 1}$$
$$C_{f1} = 3.76 \ \mu F$$

The capacitor can also be calculated by using equation:

$$C_{f1} = \frac{\left(10^{Attn/40}\right)^2}{L_f (2\pi f_{sw})^2}$$

In this case we get:

$$C_{f1} = \frac{\left(10^{28/40}\right)^2}{22 \times 10^{-6} (2 \times 3.14 \times 175 \times 10^3)^2}$$
$$C_{f1} = \frac{25.11}{22 \times 1.2 \times 10^6} = 0.95 \,\mu F$$

To satisfy both conditions, the higher value of capacitance must be selected. The selected component value is therefore 4.7uF as it is the nearest standard value.

# Selection of $C_{f2}$ and $R_{f2}$

These are the damping components used to reduce the resonant peak of the input filter. A damping capacitor is highly sensitive to the ESL of the inductor as this is the major contributor to the damping of Q in an LC filter. An electrolytic capacitor  $C_{f2}$  can also be used to reduce high output impedance at the resonant frequency. The damping capacitor and resistor are calculated as:

$$C_{f2} \ge 4 * C_{in}$$
$$R_{f2} = \sqrt{\frac{L_f}{C_{f1}}}$$



#### Test Results with Example Operating Conditions

| PARAMETER              | COMMENTS  | SPECIFICATION                          |
|------------------------|---|--|
| V <sub>ripple</sub>    | Peak noise level  | 88 dBµV                                |
| $V_{ripple(CISPR)}$    | Target noise level based on CISPR 25 Limit for Class 4 CE (with additional safety margin) | 80 (target) – 20 (safety)<br>= 68-dBµV |
| Attn                   | Required attenuation to meet target noise level   | 28-dB                                  |
| L <sub>f</sub>         | Selected LC filter inductance   | 22-µH                                  |
| $C_{f1}$ (calc)        | Calculated LC filter capacitance  | 3.76µF                                 |
| C <sub>f1</sub>        | Selected LC filter capacitance  | 4.7µF                                  |
| <i>C</i> <sub>f2</sub> | Selected damping capacitance  | 0μF                                    |

Table 2: Parameters for an undamped LC input filter design

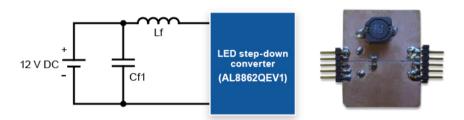


Figure 6: Undamped LC filter (a) block diagram with LED driver circuit (b) photo of the designed filter

The plot obtained using the filter under the above test conditions:

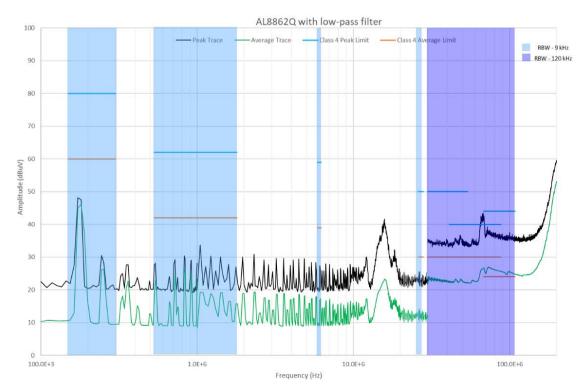


Figure 7: AL8862QEV1 with undamped LC filter, 13.5V In, 1A output current, 100 kHz – 200 MHz.



The magnitude of the attenuation level has reduced significantly from  $91dB\mu V$  to  $48dB\mu V$ , an attenuation of 43 dB $\mu V$ , after adding the undamped LC filter to the LED driver circuit. This passes CISPR 25 class 3 limits confidently and fails Class 4 at frequencies greater than 40 MHz.

### **High Frequency Attenuation**

The previous input filter is great at attenuating the lower frequencies that were causing issues, as well as attenuating differential-mode noise. However, the filter does not do a good enough job at attenuating high frequencies and does not attenuate common-mode noise at all. To help with this, a simple common-mode choke pi filter can be used to attenuate high frequencies, attenuate common-mode noise, and achieve a class 4 pass.

Shown below is a typical common-mode Pi filter. In this use case it is a simple filter with a common mode choke and two capacitors on either side.

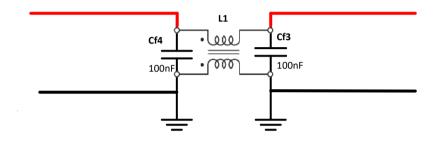


Figure 8: Common-mode Pi Filter Design

# **Component Selection:**

The 2 components needed are:

- Capacitors (C<sub>f3</sub> and C<sub>f4</sub>)
- Common-mode choke

The choice of the common-mode choke is dictated by the required attenuation frequency/frequency range and the attenuation at said frequency/frequency range. A higher impendence (Z, in  $\Omega$ ) indicates higher attenuation.

For example, for the AL8862Q, the high frequency noise problem occurs at approximately 40MHz and above. Therefore, it is best to select a common-mode choke that has a maximum impedance at anything from 40-100 MHz, and appropriate current and voltage ratings must be observed.

The Bourns SRF7035A-102Y was chosen. This part has a maximum  $Z_{(differential)}$  of 1300 $\Omega$  @ 100MHz. It also has a maximum  $Z_{(common-mode)}$  of 1000 $\Omega$  @100MHz.

To find the correct values for the capacitors, use the equation:

$$f_{c} = \frac{1}{2\pi\sqrt{L_{CM \ Choke} C_{pi}}}$$
$$C_{pi} = \frac{1}{4\pi^{2} L f_{c}^{2}}$$

Where  $f_c$  is the desired cutoff frequency,  $L_{CM Choke}$  is the inductance of the common-mode choke (available on the datasheet) and  $C_{pi}$  is the desired capacitance value. Tuning the capacitance will, by nature, alter the cutoff frequency of the common-mode choke Pi filter.



As the low pass filter is in series, to account for this simply add the capacitance value Cf1 to the equation like so:

$$f_{c} = \frac{1}{2\pi\sqrt{L_{CM \ Choke}(C_{pi} + C_{f1})}}$$
$$C_{pi} + C_{f1} = \frac{1}{4\pi^{2}Lf_{c}^{2}}$$

100nF have been chosen capacitors as they give us a cutoff frequency of approximately 26kHz. This means that the common-mode pi filter will also help with the low-frequency filtering.

Note: although the common-mode choke has a resonant frequency that amplifies the fundamental switching frequency slightly, it still has a net positive effect.

This setup produced the results shown below:

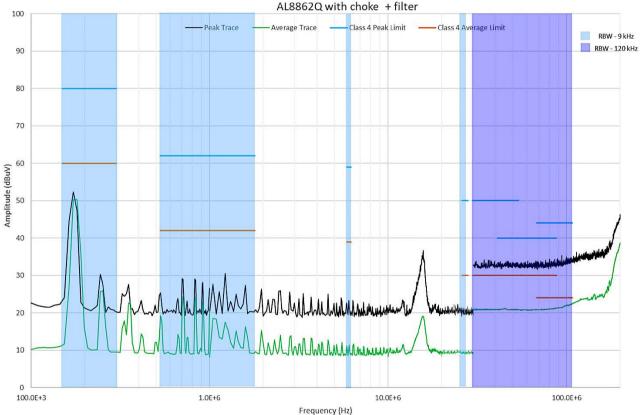


Figure 9: AL8862Q with CM Choke and Filter, 13.5V In, 1A output current, 100kHz – 200MHz

This filter setup passes class 4 confidently, with only 3 additional components.

### **Conclusion:**

This application note has shown a step-by-step method to effectively design an input filter. While we have concentrated on the AL8862QEV1 evaluation board, this methodology can be used to tackle the design of input filtering for almost any DC-DC or switching LED driver. The design of this filter is simple and yet has enabled us to improve the conducted EMC performance from exceeding CISPR 25 class 1 limits to passing class 4 limits, with reductions of as much as 40dBuV. As EMC and efficiency become increasingly important aspects of design. this methodology will help to support designers in implementing efficient switching LED drivers whilst maintaining a quiet EMC environment within the vehicle.



#### IMPORTANT NOTICE

1. DIODES INCORPORATED (Diodes) AND ITS SUBSIDIARIES MAKE NO WARRANTY OF ANY KIND, EXPRESS OR IMPLIED, WITH REGARDS TO ANY INFORMATION CONTAINED IN THIS DOCUMENT, INCLUDING, BUT NOT LIMITED TO, THE IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS (AND THEIR EQUIVALENTS UNDER THE LAWS OF ANY JURISDICTION).

2. The Information contained herein is for informational purpose only and is provided only to illustrate the operation of Diodes' products described herein and application examples. Diodes does not assume any liability arising out of the application or use of this document or any product described herein. This document is intended for skilled and technically trained engineering customers and users who design with Diodes' products. Diodes' products may be used to facilitate safety-related applications; however, in all instances customers and users are responsible for (a) selecting the appropriate Diodes products for their applications, (b) evaluating the suitability of Diodes' products for their intended applications, (c) ensuring their applications, which incorporate Diodes' products, comply the applicable legal and regulatory requirements as well as safety and functional-safety related standards, and (d) ensuring they design with appropriate safeguards (including testing, validation, quality control techniques, redundancy, malfunction prevention, and appropriate treatment for aging degradation) to minimize the risks associated with their applications.

3. Diodes assumes no liability for any application-related information, support, assistance or feedback that may be provided by Diodes from time to time. Any customer or user of this document or products described herein will assume all risks and liabilities associated with such use, and will hold Diodes and all companies whose products are represented herein or on Diodes' websites, harmless against all damages and liabilities.

4. Products described herein may be covered by one or more United States, international or foreign patents and pending patent applications. Product names and markings noted herein may also be covered by one or more United States, international or foreign trademarks and trademark applications. Diodes does not convey any license under any of its intellectual property rights or the rights of any third parties (including third parties whose products and services may be described in this document or on Diodes' website) under this document.

5. Diodes' products are provided subject to Diodes' Standard Terms and Conditions of Sale (<u>https://www.diodes.com/about/company/terms-and-conditions/terms-and-conditions-of-sales/</u>) or other applicable terms. This document does not alter or expand the applicable warranties provided by Diodes. Diodes does not warrant or accept any liability whatsoever in respect of any products purchased through unauthorized sales channel.

6. Diodes' products and technology may not be used for or incorporated into any products or systems whose manufacture, use or sale is prohibited under any applicable laws and regulations. Should customers or users use Diodes' products in contravention of any applicable laws or regulations, or for any unintended or unauthorized application, customers and users will (a) be solely responsible for any damages, losses or penalties arising in connection therewith or as a result thereof, and (b) indemnify and hold Diodes and its representatives and agents harmless against any and all claims, damages, expenses, and attorney fees arising out of, directly or indirectly, any claim relating to any noncompliance with the applicable laws and regulations, as well as any unintended or unauthorized application.

7. While efforts have been made to ensure the information contained in this document is accurate, complete and current, it may contain technical inaccuracies, omissions and typographical errors. Diodes does not warrant that information contained in this document is error-free and Diodes is under no obligation to update or otherwise correct this information. Notwithstanding the foregoing, Diodes reserves the right to make modifications, enhancements, improvements, corrections or other changes without further notice to this document and any product described herein. This document is written in English but may be translated into multiple languages for reference. Only the English version of this document is the final and determinative format released by Diodes.

8. Any unauthorized copying, modification, distribution, transmission, display or other use of this document (or any portion hereof) is prohibited. Diodes assumes no responsibility for any losses incurred by the customers or users or any third parties arising from any such unauthorized use.

9. This Notice may be periodically updated with the most recent version available at <a href="https://www.diodes.com/about/company/terms-and-conditions/important-notice">https://www.diodes.com/about/company/terms-and-conditions/important-notice</a>

The Diodes logo is a registered trademark of Diodes Incorporated in the United States and other countries. All other trademarks are the property of their respective owners. © 2024 Diodes Incorporated. All Rights Reserved.

#### www.diodes.com