

# AN1182

## DGD2388M Application Note

David Toro, Bipolar Business Unit, Diodes Incorporated

The DGD2388M is a highly integrated three-phase gate driver IC used to drive N-Channel MOSFETs or IGBTs. Below (Figure 1) is an example application of using the DGD2388M with IGBTs to make three half-bridge circuits used to drive a three-phase motor; typical motor applications are AC Induction motors, PMSMs, and BLDC motors. In this discussion, the important parameters needed to design in the DGD2388M are discussed; main sections are bootstrap resistor, diode, and capacitor selection, gate driver component selection, and decoupling capacitor value.

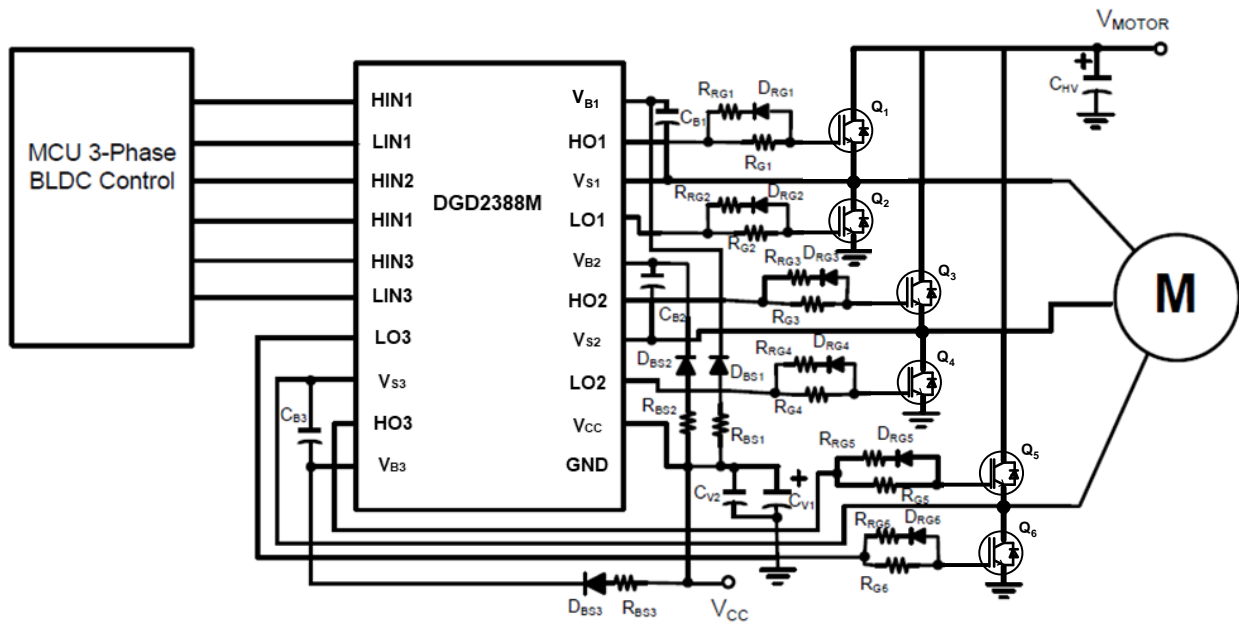


Figure 1. Application example of DGD2388M

# Bootstrap Component Selection

## Bootstrap Resistor

Considering Figure 1, when the Low-Side IGBT (Q2, Q4, or Q6) turns on,  $V_S$  pulls to GND and the bootstrap capacitor ( $C_{B1}$ ,  $C_{B2}$ , and  $C_{B3}$ ) is charged. When the High-Side IGBT (Q1, Q3, and Q5) is turned on,  $V_S$  swings above  $V_{CC}$  and the charge on the bootstrap capacitor ( $C_B$ ) provides current to drive the IC High-Side gate driver. The first charge of  $C_B$  from  $V_{CC}$  through the bootstrap resistor ( $R_{BS1}$ ,  $R_{BS2}$ , and  $R_{BS3}$ ) and bootstrap diode ( $D_{BS1}$ ,  $D_{BS2}$ , and  $D_{BS3}$ ) occurs when power is first applied, and Low-Side turns on the first time. At this time, the charge current is the largest, as typically  $C_B$  is not discharged fully at each cycle.

A bootstrap resistor ( $R_{BS}$ ) is included in the bootstrap circuit to limit the inrush current that charges  $C_B$  when  $V_S$  pulls below  $V_{CC}$ ; this inrush current is largest with the first charge. Limiting inrush current is desirable to limit noise spike on  $V_S$  and COM, potentially causing shoot-through. The amplitude and length of time of the inrush current is determined mostly by the component value of  $R_{BS}$  and  $C_B$  as well as  $V_{CC}$  level. The aim in resistor selection for the application is to slow down the inrush current but have minimal effect on the  $R_C$  time constant of charging  $C_B$ .

Typically, values for  $R_{BS}$  are  $3\Omega$  to  $10\Omega$ , enough to dampen the inrush current but have little effect on the  $V_{BS}$  turn on. Below are some scope shots illustrating the effect of different  $R_{BS}$  values.

 


Figure 2. Bootstrap inrush current with  $R_{BS} = 3\Omega$ ,  $C_B = 2.2\mu F$

 


Figure 3. Bootstrap inrush current with  $R_{BS} = 10\Omega$ ,  $C_B = 2.2\mu F$

 


Figure 4.  $V_{BS}$  rise time ( $11.8\mu s$ ) with  $C_B = 2.2\mu F$  and  $R_{BS} = 3\Omega$  resistor

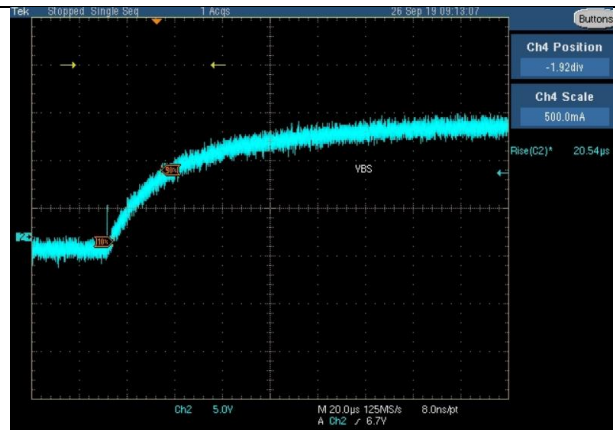


Figure 5.  $V_{BS}$  rise time ( $20.5\mu s$ ) with  $C_B = 2.2\mu F$  and  $R_{BS} = 10\Omega$  resistor

## Bootstrap Diode

The chosen bootstrap diode ( $D_{BS}$ ) should be rated higher than the maximum rail voltage since the diode must be able to block the full rail voltage and any spikes seen at the  $V_S$  node. The diode's current rating is simply the product of total charge ( $Q_T$ ) required by the HVIC and the switching frequency. An ultrafast recovery diode is recommended to minimize any delay of charging the bootstrap capacitor  $C_B$ . A 1A ultrafast recovery diode is typical for DGD2388M applications.

## Bootstrap Capacitor

The initial step in determining the value of the bootstrap capacitor is to determine the minimum voltage drop ( $\Delta V_{BS}$ ) that can be guaranteed when the High-Side device is turned on. In other words, the minimum gate-source voltage ( $V_{GSmin}$ ) must be greater than the UVLO of the High-Side circuit, specifically  $V_{BSUV}$  level. Therefore, if  $V_{GSmin}$  is the minimum gate-source voltage such that:  
 $V_{GSmin} > V_{BSUV}$ .

Then:

$$\Delta V_{BS} = V_{CC} - V_F - V_{GSmin} - V_X$$

Where:

- $V_{CC}$  is the supply voltage to the DGD2388M
- $V_F$  is the voltage drop across the bootstrap diode ( $D_{BS}$ )
- $V_X$  is the voltage drop across the MOSFET or IGBT

$V_X$  is calculated as the current seen across Low-Side MOSFET multiplied by its  $R_{DS(on)}$  and is simply  $V_{CE-ON}$  at the specify output current if an IGBT were used instead.

In addition to the voltage drops across these components, other factors that cause  $V_{BS}$  to drop are leakages, charge required to turn on the power devices, and duration of the High-Side on time. The total charge ( $Q_T$ ) required by the gate driver then equals:

$$Q_T = Q_G + Q_{LS} + [I_{LK\_N}] * T_{HON}$$

Where:

$Q_G$  = Gate charge of power device

$Q_{LS}$  = Level shift charge required per cycle

$T_{HON}$  = High-Side on time

$I_{LK\_N}$  = Sum of all leakages that include:

- $I_{GSS}/I_{GES}$ : Gate-source leakage of the power device
- $I_{LK\_DB}$ : Bootstrap diode leakage
- $I_{LK\_IC}$ : Offset supply leakage of HVIC
- $I_{QBS}$ : Quiescent current for High-Side supply
- $I_{LK\_CBS}$ : Bootstrap capacitor leakage

Bootstrap capacitor leakage ( $I_{LK\_CBS}$ ) only applies to electrolytic types. Therefore, it is best not to use electrolytic capacitor. Thus, bootstrap capacitor leakages will not be included in the calculations.

$Q_{LS}$  is not listed in the datasheet; depending on the process technology, it could range anywhere from 3nC – 20nC for 500V to 1200V process respectively. Assuming a value of 10nC for Diode's 600V, this process should be sufficient with added margin.

From the basic equation, the minimum bootstrap capacitor can be calculated as:

$$C_{Bmin} \geq Q_T / \Delta V_{BS}$$

### Example using IGBT

- Power device: IRGB4066
- HVIC = DGD2388M
- $V_{CC} = 15V$
- $I_{out} = 40A$
- $T_{HON} = 50\mu s$
- $V_{CE-max} = \sim 2.0V$
- $Q_G = 225nC$
- $I_{GSS}/I_{GES} = 200nA$
- $I_{LK\_DB} = 100\mu A$
- $I_{LK\_IC} = 10\mu A$
- $I_{QBS} = 130\mu A$

From equations above:

$$\Delta V_{BS} = 15V - 3.0V - 4V - 2.0V = 6.0V$$

$$\begin{aligned} Q_T &= Q_G + Q_{LS} + (I_{LK\_N} * T_{HON}) \\ &= 225nC + 10nC + 12nC \\ &= 247nC \end{aligned}$$

Thus,  $C_B \text{ min} = 254\text{nC}/6\text{V} = 41.2\text{nF}$

The bootstrap capacitor calculated in the above problem is the minimal value required to supply the needed charge. It is recommended that a margin of 2 – 3 times the calculated value be used. In addition, if the added margin is significantly small still such that it is lower than  $0.47\mu\text{F}$ , the minimal value should be brought up to this value. Utilizing values lower than this could result in over-charging of the bootstrap capacitor especially during  $-V_S$  transients. Typically for motor driver applications  $C_B = 1\mu\text{F}$  to  $10\mu\text{F}$  are used; it is also recommended to use low ESR ceramic capacitors as close to the  $V_B$  and  $V_S$  pin as possible (see PCB layout suggestions section).

## Gate Resistor Component Selection

The most crucial time in the gate drive is the turn on and turn-off of the MOSFET, and performing this function quickly, but with minimal noise and ringing is key. Too fast a rise/fall time can cause unnecessary ringing and poor EMI, and too slow a rise/fall time will increase switching losses in the MOSFET.

 


Figure 6. Phase1 gate drive components for DGD2388M

Considering the phase 1 gate driver components for DGD2388M in Figure 6, with the careful selection of  $R_{G1}$  and  $R_{RG1}$ , it is possible to selectively control the rise time and fall time of the gate drive. For turn on, all current will go from the IC through  $R_{G1}$  and charge the IGBT gate capacitor, hence increasing or decreasing  $R_{G1}$  will increase or decrease rise time in the application. With the addition of  $D_{RG1}$ , the fall time can be separately controlled as the turn off current flows from the MOSFET gate capacitor, through  $R_{RG1}$  and  $D_{RG1}$  to the driver in the IC to  $V_S$ . So, increasing or decreasing  $R_{RG1}$  will increase or decrease the fall time. Sometimes finer control is not needed and only  $R_{G1}$  is used.

Increasing turn on and turn off has the effect of limiting ringing and noise due to parasitic inductances, hence with a noisy environment, it may be necessary to increase the gate resistors. Gate component selection is a compromise of faster rise time with more ringing, and a poorer EMI but better efficiency, and a slower rise time with better EMI, better noise performance, but poorer efficiency. The exact value depends on the parameters of the application. Generally, for motors the switching speed is slower, and the application has more inherent noise, higher values are recommended, for example  $R_G = 20\Omega - 100\Omega$ .

## Decoupling Capacitor Selection

For optimal operation,  $V_{CC}$  decoupling is crucial for all gate driver ICs including the DGD2388M; with poor decoupling,  $V_{CC}$  can drop when switching and for greater  $V_{CC}$  drop the IC can go into UVLO. In the configuration shown in Figure 1, two decoupling capacitors are recommended  $C_{V1}$  and  $C_{V2}$  (see Figure 7), both connected from  $V_{CC}$ -GND.  $C_{V1}$  can be a larger electrolytic, for example  $47\mu\text{F}$ ,  $50\text{V}$  and does not need to be right next to the IC. But  $C_{V2}$  should be a low ESR ceramic capacitor placed close to the  $V_{CC}$  pin. This component provides stability when  $V_{CC}$  is quickly pulled down with load; typical values are  $0.1\mu\text{F}$  to  $1\mu\text{F}$ .

 


Figure 7. Decoupling capacitors on the DGD2388M

## Matching Gate Driver with MOSFET or IGBT

### IC drive current and MOSFET/IGBT gate charge

Gate Driver ICs are defined by their output drive current, its ability to source current to the gate of the MOSFET/IGBT at turn on and to sink current from the gate of the MOSFET/IGBT at turn off. For the DGD2388M the drive current is  $I_{O+}=420\text{mA}$  typical and  $I_{O-}=750\text{mA}$  typical.

For a given MOSFET/IGBT, with the known drive current of the DGD2388M, you can calculate how long it will take to turn on/off the MOSFET/IGBT with the equation:

$$t = Q_g / I$$

$Q_g$  = total charge of the MOSFET/IGBT as provided by the datasheet

$I$  = sink/source capability of the gate driver IC

$t$  = calculated rise/fall time with the given charge and drive current

For example, with Diodes Incorporated's (Diodes) DGTD65T15H2TF, 650V IGBT,  $Q_g = 61\text{nC}$ ; and with the DGD2388M  $I_{O+}/I_{O-}$ ,  $t_r = 145\text{ns}$  and  $t_f = 81\text{ns}$ . These are estimates as the total charge given in the datasheet may not be the same conditions in the application. Also, an addition of a gate resistor will increase the  $t_r$  and  $t_f$ .

## MOSFET/IGBT Input Capacitance Ratio

In the half-bridge circuit (see Figure 8), when the Low-Side turns on,  $V_s$  swings low at a rate of  $dV_s/dt$ . Depending on the  $dV_s/dt$  of the system, and a ratio of  $C_{ies}/C_{res}$  of the IGBT, there can be an inadvertent turning on the High-Side IGBT during this transition; if this occurs shoot through will happen, possibly damaging the IGBT and causing inefficiency. Often, this is the reason for short unexplained shoot through. If this is the case, another IGBT with larger  $C_{ies}/C_{res}$  should be chosen, or a capacitor (for example 1nF) can be added between the gate and emitter of the IGBTs.

 


Figure 8. Half-bridge with High-Side IGBT equivalent capacitors

## Minimum Pulse Requirement

The DGD2388M has a typical propagation delay of 120ns. With the prop delay of the DGD2388M, delay time from gate resistors, and rise/fall from the MOSFETs/IGBTs, for optimal operation, it is suggested to provide a minimum pulse width at the input to the IC from the MCU. As a rule of thumb, this minimum pulse should be 2x deadtime or 660ns.

## PCB Layout Suggestions

Layout plays an important role in minimizing unwanted noise coupling, unpredicted glitches, and abnormal operation which can arise from poor layout. Figure 9 shows a single-phase half-bridge schematic with parasitic inductances in the high current path ( $L_{P1}$ ,  $L_{P2}$ ,  $L_{P3}$ ,  $L_{P4}$ ) which would be caused by inductance in the metal of the trace. Considering Figure 9, the length of the tracks in red should be minimized, and the bootstrap capacitor ( $C_B$ ) and the decoupling capacitor ( $C_D$ ) should be placed as close to the IC as possible as well as using low ESR ceramic capacitors. Finally, the gate resistors ( $R_{GH}$  and  $R_{GL}$ ) and the sense resistor ( $R_S$ ) should be surface mount devices. These suggestions will reduce the parasitics due to the PCB traces.

 


Figure 9. Layout suggestions for single phase of three-phase system

 


Figure 10. Layout of the schematic shown in Figure 1, DGD2388M in SOIC20, IGBTs in TO220 packages.

## IMPORTANT NOTICE

1. DIODES INCORPORATED (Diodes) AND ITS SUBSIDIARIES MAKE NO WARRANTY OF ANY KIND, EXPRESS OR IMPLIED, WITH REGARDS TO ANY INFORMATION CONTAINED IN THIS DOCUMENT, INCLUDING, BUT NOT LIMITED TO, THE IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS (AND THEIR EQUIVALENTS UNDER THE LAWS OF ANY JURISDICTION).

2. The Information contained herein is for informational purpose only and is provided only to illustrate the operation of Diodes' products described herein and application examples. Diodes does not assume any liability arising out of the application or use of this document or any product described herein. This document is intended for skilled and technically trained engineering customers and users who design with Diodes' products. Diodes' products may be used to facilitate safety-related applications; however, in all instances customers and users are responsible for (a) selecting the appropriate Diodes products for their applications, (b) evaluating the suitability of Diodes' products for their intended applications, (c) ensuring their applications, which incorporate Diodes' products, comply the applicable legal and regulatory requirements as well as safety and functional-safety related standards, and (d) ensuring they design with appropriate safeguards (including testing, validation, quality control techniques, redundancy, malfunction prevention, and appropriate treatment for aging degradation) to minimize the risks associated with their applications.

3. Diodes assumes no liability for any application-related information, support, assistance or feedback that may be provided by Diodes from time to time. Any customer or user of this document or products described herein will assume all risks and liabilities associated with such use, and will hold Diodes and all companies whose products are represented herein or on Diodes' websites, harmless against all damages and liabilities.

4. Products described herein may be covered by one or more United States, international or foreign patents and pending patent applications. Product names and markings noted herein may also be covered by one or more United States, international or foreign trademarks and trademark applications. Diodes does not convey any license under any of its intellectual property rights or the rights of any third parties (including third parties whose products and services may be described in this document or on Diodes' website) under this document.

5. Diodes' products are provided subject to Diodes' Standard Terms and Conditions of Sale (<https://www.diodes.com/about/company/terms-and-conditions/terms-and-conditions-of-sales/>) or other applicable terms. This document does not alter or expand the applicable warranties provided by Diodes. Diodes does not warrant or accept any liability whatsoever in respect of any products purchased through unauthorized sales channel.

6. Diodes' products and technology may not be used for or incorporated into any products or systems whose manufacture, use or sale is prohibited under any applicable laws and regulations. Should customers or users use Diodes' products in contravention of any applicable laws or regulations, or for any unintended or unauthorized application, customers and users will (a) be solely responsible for any damages, losses or penalties arising in connection therewith or as a result thereof, and (b) indemnify and hold Diodes and its representatives and agents harmless against any and all claims, damages, expenses, and attorney fees arising out of, directly or indirectly, any claim relating to any noncompliance with the applicable laws and regulations, as well as any unintended or unauthorized application.

7. While efforts have been made to ensure the information contained in this document is accurate, complete and current, it may contain technical inaccuracies, omissions and typographical errors. Diodes does not warrant that information contained in this document is error-free and Diodes is under no obligation to update or otherwise correct this information. Notwithstanding the foregoing, Diodes reserves the right to make modifications, enhancements, improvements, corrections or other changes without further notice to this document and any product described herein. This document is written in English but may be translated into multiple languages for reference. Only the English version of this document is the final and determinative format released by Diodes.

8. Any unauthorized copying, modification, distribution, transmission, display or other use of this document (or any portion hereof) is prohibited. Diodes assumes no responsibility for any losses incurred by the customers or users or any third parties arising from any such unauthorized use.

9. This Notice may be periodically updated with the most recent version available at <https://www.diodes.com/about/company/terms-and-conditions/important-notice>

The Diodes logo is a registered trademark of Diodes Incorporated in the United States and other countries.  
All other trademarks are the property of their respective owners.  
© 2023 Diodes Incorporated. All Rights Reserved.

[www.diodes.com](http://www.diodes.com)