

PI3DSB12212A application information

Table of Contents

| | | |
|---|-----------------------------------|---|
| 1 | Introduction | 2 |
| 2 | Typical Application Circuit..... | 2 |
| 3 | Main Link Channels | 3 |
| 4 | Control Pins..... | 3 |
| 5 | Differential insertion loss | 4 |
| 6 | Layout and power | 5 |

1. Introduction

Thunderbolt, SAS 3.0, USB3.1, PCIe G3 and many protocol new revisions request a switch with bandwidth up to 12Gbps, such as PI3DBS12212A.

2. Typical Application Circuit

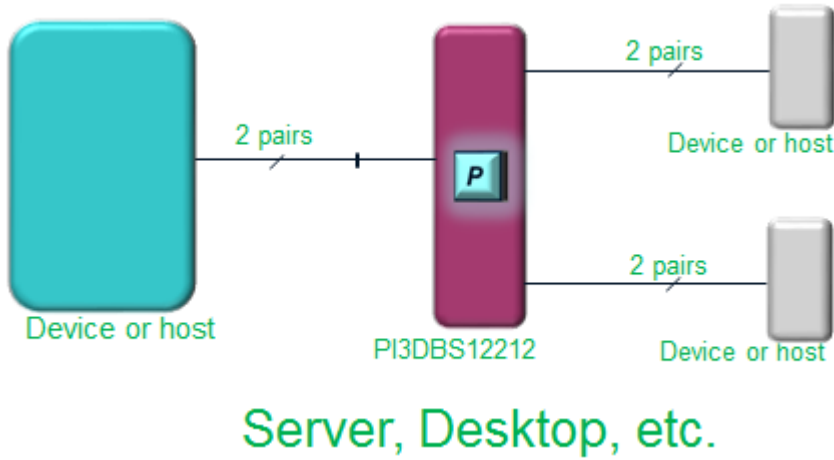


Figure 1: PI3DBS12212A application topologie

|

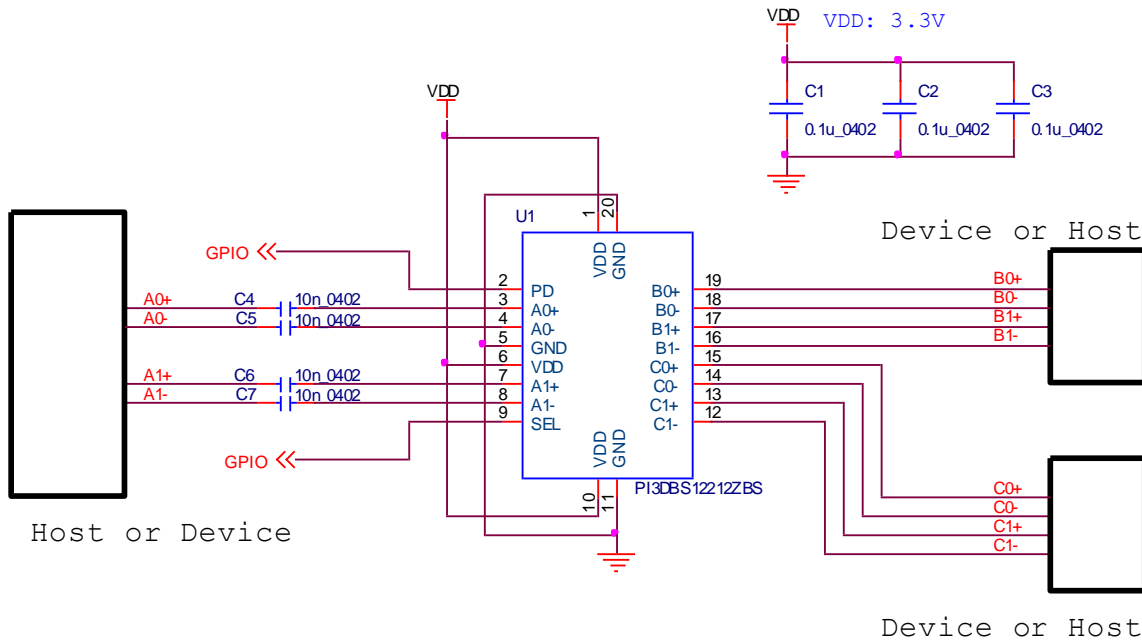


Figure 2, PI3DBS1221AZBS@TQFN20 application schematic

3. Main Link Channels

In applications (figure 1, 2, 3), AC coupling capacitors can be either between host-PI3DBS1221A or between device-PI3DBS1221A.

Assure the signals going thru PI3DBS1221A is in the range of -0.5V to 1.6V single-ended, which is the allowable working voltage range of PI3DBS1221A.

4. Control Pins

OE1# and OE2# pins can be tied to ground. Use a system GPIO to control SEL pin.

5. Differential insertion loss

Figure-4 is the differential insertion loss of PI3DBS1221A.



Figure-4, the -1.2493db /5.646Ghz (11.2Gbps) differential insertion loss of PI3BDS12412A (reference for PI3BDS12212A)

6 Layout and power

90ohm differential impedance

| Plane | Material | Thickness (mil) |
|-------------|------------|-----------------|
| Solder mask | Mask paint | 1.2 |
| Signal | Copper | 1.9 |
| Prepreg | 2116 | 4.4 |
| Vcc | Copper | 1.4 |
| Core | | 47 |
| Vss | Copper | 1.4 |
| Prepreg | 2116 | 4.4 |
| Signal | Copper | 1.9 |
| Solder mask | Mask paint | 1.2 |
| Total | | 62.4 |

Table-2, the stack-up of 90ohm differential impedance

- ❑ Use 6-7-6 mils for trace-space-trace for the micro-strip lines (the traces on top and bottom layers) for 90ohm differential impedance.
- ❑ Use 6-5-6 mils for trace-space-trace for the strip-lines (the traces inside layers) for 90ohm differential impedance.

- ❑ Use FR4.
- ❑ Using standard 4 to 8 layers stack-up with 0.062 inch thick PCB.
- ❑ For micro-strip lines, using ½ OZ Cu plated is ok.
- ❑ For strip-lines in 6 plus players, using 1 OZ Cu is better.
- ❑ More pair-to-pair spacing for minimal crosstalk
- ❑ Target differential Z_0 of 90ohm \pm 15ohm
- ❑ The above is only for generic reference. Impedance shall be controlled in PCB fabrication.

 


Figure 13, the PCB layers stack-up

The layout of traces

 


Figure 14, the layout of traces

VDD bypass capacitance and power-ground layers

- Use 0.1uf in size of 0402 for all the VDD (any power pins) pins of the IC device, as close to the VDD pins as possible, within 2-3mm if feasible.
- Use dedicated VDD and GND planes if feasible to minimize the power noise.