

General Description

Based on Flyback topology, the Primary side Regulated AP3983E EV1 board is designed to serve as an example for High Efficiency, low cost & less components consumer home appliance systems. Also a 700V N MosFet is integrated within control IC for easy fitting in a flexible & small size power system design. During the valley on operating & work at PFM region the high efficiency and low standby function can be achieved, by mean of using multi-mode controlling skill the accurate constant voltage and constant current can be easy meet. Its output power is rated at 18W with 12V-1.5A. It can meet DOE VI and CoC Tier 2 energy efficiency requirement.

Key Features

- 90 ~264V_{AC} input range
- Using the Primary side control for eliminating the Opto-coupler.
- Multi-Mode PFM method operations, the switching frequency between 24kh ~80Khz.
- With Valley on detection the switching stay at Valley on region so that will improve power converting efficiency & EMI performance, the 86% Efficiency can be reached at full load.
- During the burst mode operation and Low startup operating quiescent currents the 75mW low standby input power can be achieved.
- Dynamic response is improved during work at three mode operation as well as benefiting the accurate constant voltage (CV) regulation & constant current (CC) performance.
- There is a Soft start during startup process.
- Built-in Jittering Frequency function which is the EMI emission can be improved.
- Internal Auto Recovery OCP, OVP, OLP, OTP Power Protection, cycle by cycle current limit, also with DC polarity protection
- Built -in Cable Compensation mode.
- With a Brown out Protection.

Applications

- Switching AC-DC Adaptor & Charger
- Power home Appliances systems
- Set-top box & ADSL or small wireless Router system
- The auxiliary Vcc power supply for bigger power system.

Universal AC input PSR 12V-1.5A Power Specifications (CV & CC mode)

Parameter	Value
Input Voltage	90 to 264V _{AC}
Input standby power	75mW
Main output Vo / Io	12V – 1.5A
Efficiency	~ 86%
Total Output Power	18W
Protections	OCP, OVP, OLP,OTP
XYZ Dimension	50.4.0 x 50.4 x 25 mm
ROHS Compliance	Yes

Evaluation Board Picture:



Figure 1: Top View

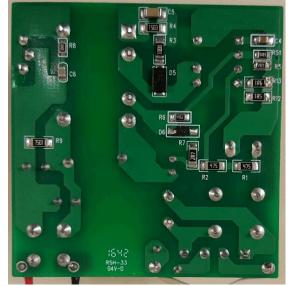



Figure 2: Bottom View



AP3301 (90 V_{AC} ~ 265 V_{AC} one outputs 42W Transformer Spec.)

1) Core & Bobbin: EE25, 5+5 pin

2) Electrical Diagram:

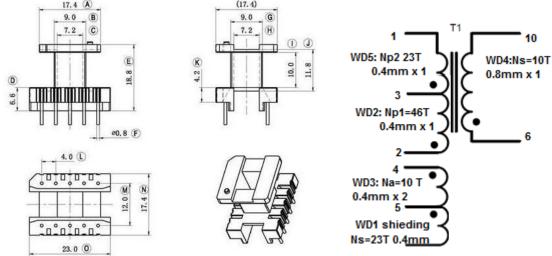

3) Transformer Parameters

1. Primary Inductance (Pin2-Pin1), all other windings are open $Lp = 0.70mH \pm 7\%$ @1KHz

RM8 (RM8 (Ae = 64mm^2)					
NO		TERMINAL NO.		WINDING		
Winding NAME		START	FINISH	WIRE	TURNS	Layers
1	Np1	2	3	Φ 0.4mm	46Ts	2
2	Na	4	5	Φ 0.4mm x 2	10 Ts	1
3	Shield	5 (GND)	NC	Ф 0.4mm x 1	23T	1
4	Ns	10(+)	6	Ф 0.8W х 1	10 Ts	1
5	Np2	3	1	Ф 0.35 (27# AWG)	23	1
Primary Ir	Primary Inductance Pin 2-1,all other windings open, measured at 1kHz, 0.4VRMS 700uH ± 7 %				7 %	

Primary Leakage Inductance

Pin 2-1, all other windings shorted, measured at 10kHz, 0.4VRMS

80 uH (Max.)

Evaluation Board Schematic

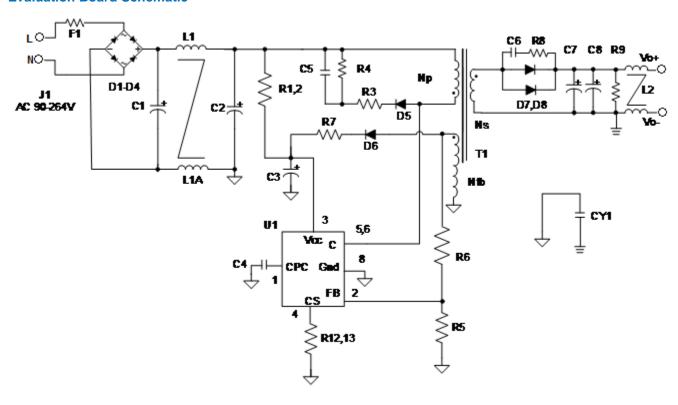


Figure 3: Evaluation Board Schematic

Evaluation Board PCB Layout

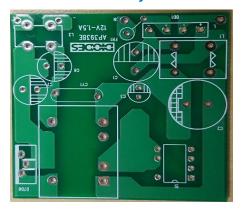


Figure 4: PCB Board Layout Top View

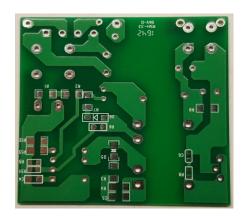


Figure5: PCB Board Layout Bottom View



Quick Start Guide

- 1. The evaluation board is preset at 12V/1.5A from output + & -
- 2. Ensure that the AC source is switched OFF or disconnected before doing connection.
- 3. Connect the AC line wires of power supply to "L and N" on the left side of the board.
- 4. Turn on the AC main switch.
- 5. Measure Red & Black wires to ensure correct output voltages at 12V respectively.

Build of Material

AP3983E 12V-1.5A BOM 10-19-2016

	Item	QTY per	REF. DES.	Description	MFG or Supplier	MFG P/N or Supplier P/N Digi key #
ı	1	1	C1	22uf /400V 10 x 18mm	Wurth Electro	
	2	2	C2	47uf /400V 12.5 x 20mm	Wurth Electro	
	3	1	C3	3.3uf/50V E-cap	Wurth Electro	
	4	1	C4	10 nF/50V 0805 ceramic	Yageo	
	5	1	C5	2.2nf / 500V, 0805 X7R	Holy Stone	
	6	1	C6	1nf 250V 0805 X7R	Holy Stone	
	7	2	C7 & C8	680nf /16V E-cap	Wurth Electro	
	8	2	R1, R2	4.7M ohm 1206	Yageo	
	9	1	R3	100R hom 1206	Yageo	
	10	1	R4	150kohm 1206	Yageo	
	11	2	R5 //R51	22.6k //510k ohm 0805	Yageo	
	12	1	R6	47.5K ohm 0805	Yageo	
	13	1	R7	2.7R ohm, 0805	Yageo	
	14	1	R8	30R ohm, 1206	Yageo	
	15	1	R9	7.5K ohm 1206	Yageo	
	16	2	R12, R13	1.5R//1.6R ohm 1206	Yageo	
	17		R10	off	_	
	18	1	BD1	KBP206G	Diodes 2A-600V	
	19	2	D5, D6		Diodes 1A-600V	
	20	1	D7, D8	SDT20B100	Diodes 10A/100V	
	21	1	F1	1.25A/250V		
	22	1	UU9.8 22mH	22mH common mode chock	Wurth Electro	
	23	1	CY1	1000pf/250Vac Y1	Holy Stone	
	24	1	IC	AP3983E DIP-7	Diodes	



Input & Output Characteristics

Input Standby Power

Input Voltage	115Vac/60Hz	230Vac/50Hz	Note
Pin (w)	52mW	69mW	At no loading

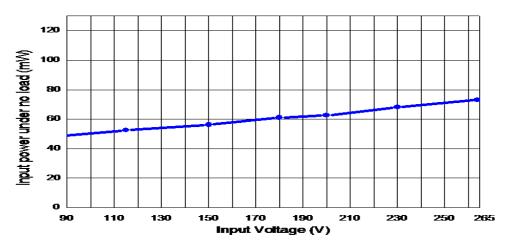


Figure 6: The Efficiency curve with at different AC input

Input power Efficiency at different loading

AC input	Efficiency (%)					Eff_avg at four
AC input	10%	25%	50%	75%	100%	conditions
90VAC/60Hz					84.7%	
115VAC/60Hz	79.8%	84.6.0%	85.8%	85.8%	85.6%	85.5%
230VAC/50Hz	79.05%	82.5%	86.6%	86.8%	86.2%	85.5%
264VAC/50Hz					86.1%	
Eff_avg						

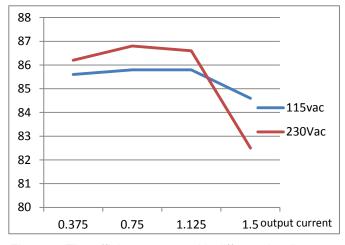


Figure 7: The efficiency curve with different loading

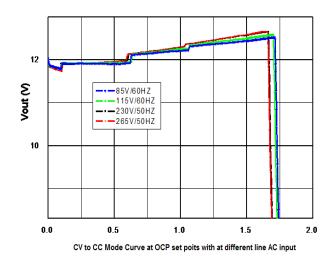


Figure 8: CV & CC Curve at OCP set poits

OCP Current set point with at different AC line

AC input	90VAC	115VAC	230VAC	264VAC	Note
I _max	1.67A	1.68A	1.72A	1.74A	

PSU Output Characteristics:

Line Regulation (at full loading condition):

AC input Voltage	90Vac/60Hz	115VAC/60Hz	230VAC/50Hz	265VAC/50Hz	Note
12.00Vo	12.16V/1.5A	12.19V/1.5A	12.24V/1.5A	12.26V/1.5A	0.82%<1%

Cross Load Regulation (at nominal line AC input voltage):

AC input Voltage	115VAC/60Hz	230VAC/50Hz
12V Full Load	12.19V / 1.5A	12.24V/1.5A
12V 10% of FL	11.61V /0.15A	11.59V/0.15A
Note	4.8%	5.5%

Note: All output voltages are measured at output PCB board Edge.

Key Performance Waveforms:

System start - up time

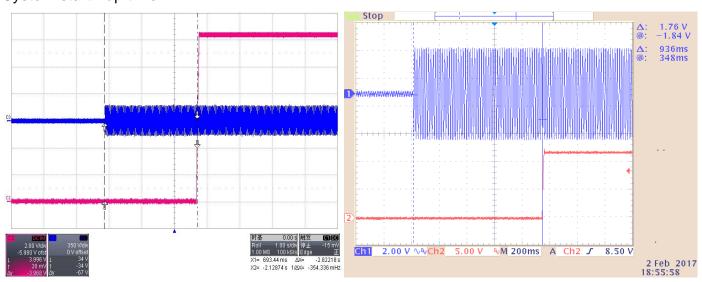


Figure 9:AP3983E turn on time 2.8sFL at 90Vac

Figure 10: AP3983E turn on time 0.94s at FL, at 230Vac



System main switching Voltage Stress on AP3983E Pin 5&6

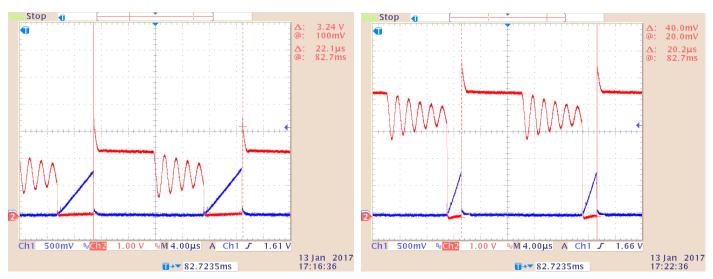


Figure 11:AP3983E Vds at FL at 100Vac Vds=140Vp-p

Figure 12: AP3983E Vds at FL at 264 Vac, Vds=570Vp-p

System Voltage Stress across on Q2 D-S

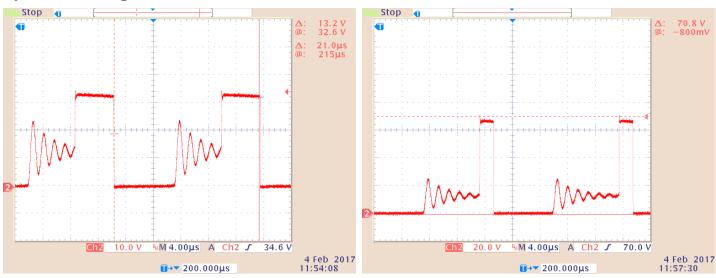


Figure 13: Q2 D-S voltage stress at 100Vac FL $Vq2 d_S = 34Vp-p 10V/div$

Figure 14: Q2 D-S voltage stress at 264Vac at FL $Vq2 d_S = 71Vp-p 20V/div$



System output Ripple performance

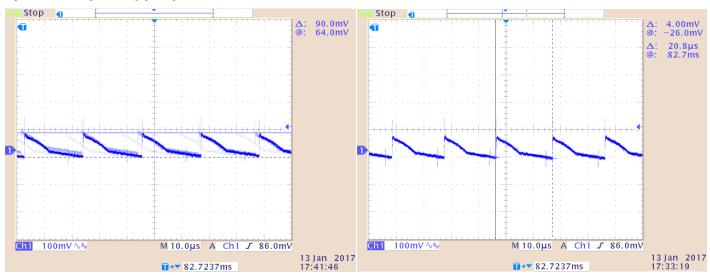


Figure 15: The Ripple at 100Vac_in Vpp=90mv FL

Figure 16: The Ripple at 230Vac_in Vpp=83mv FL

System Dynamic Response performance

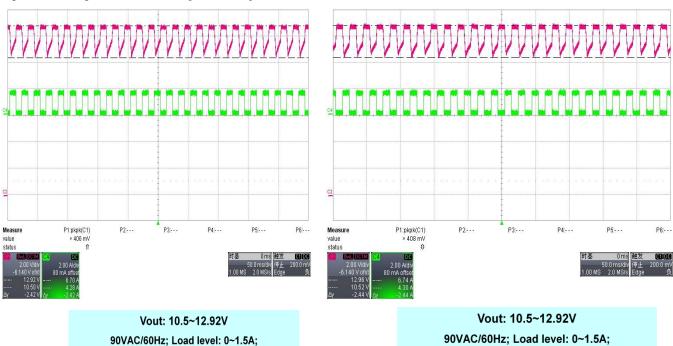


Figure 17: Frequency: 10mS-10mS. Slew rate: 250A/us

Figure 18:

90VAC/60Hz; Load level: 0~1.5A; Frequency: 10mS-10mS. Slew rate: 250A/us



System Dynamic Response performance


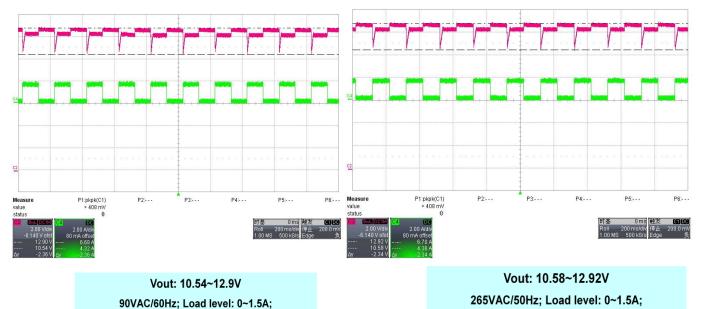


Figure 19:

Figure 20:

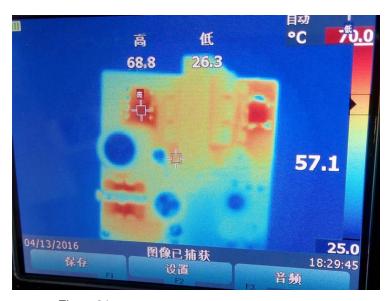Thermal Test data at room Temperature after running 1 hr




Frequency: 100mS-100mS. Slew rate: 250A/us



90VAC/50Hz, lout=1.5A

T_{A=25°} AP3983E surface = 68.8°

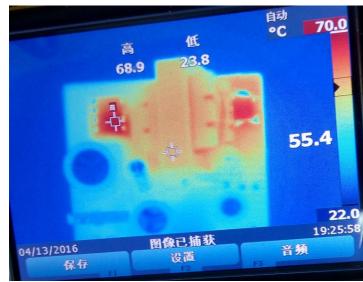

Frequency: 100mS-100mS. Slew rate: 250A/us

Figure22:

264VAC/50Hz, lout=1.5A

T_{A=22°} AP3983E Surface T=68.9°



System EMI L-Line Scan Data

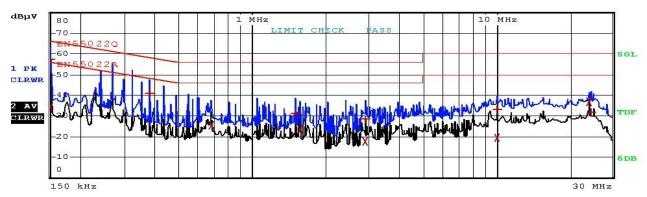


Figure 23: EMI Scan at 115Vac

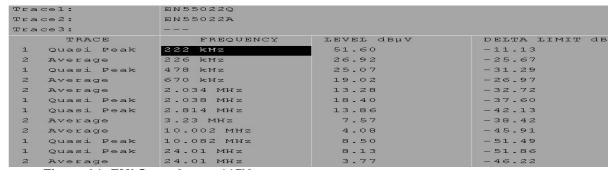


Figure 24: EMI Scan data at 115Vac

System EMI N-Line Scan Data

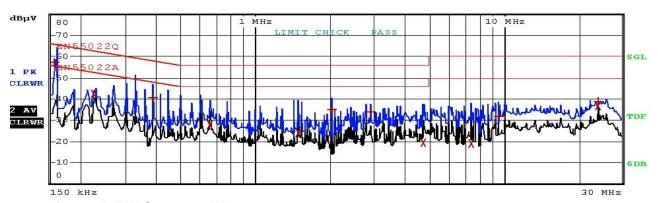


Figure 25: EMI Scan at 115Vac



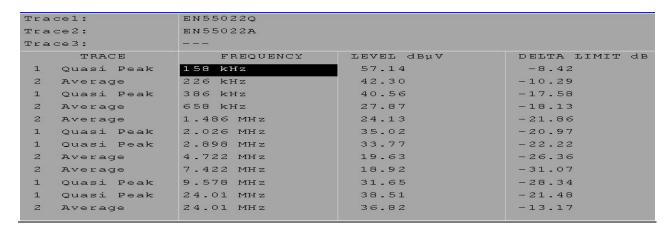


Figure 26: EMI Scan data at 115Vac

Please see the recommand Application note for reference (Web page - http://www.diodes.com/appnote_dnote.html)

- For AP3125 operation & set up, please review the Application note: Application note 1120 Green Mode PWM Controller
- 2) For PSU PCB layout consideration, please review the App note: AN1062 High Voltage Green Mode PWM Controller AP3105
- For the basic Flyback topology calculation, please review the App note: AN1045 Design Guidelines for Off-line AC-DC Power Supply Using BCD. PWM Controller AP3103



IMPORTANT NOTICE

DIODES INCORPORATED MAKES NO WARRANTY OF ANY KIND, EXPRESS OR IMPLIED, WITH REGARDS TO THIS DOCUMENT, INCLUDING, BUT NOT LIMITED TO, THE IMPLIED WARRANTIES OF MERCHANTABILITY AND FITNESS FOR A PARTICULAR PURPOSE (AND THEIR EQUIVALENTS UNDER THE LAWS OF ANY JURISDICTION).

Diodes Incorporated and its subsidiaries reserve the right to make modifications, enhancements, improvements, corrections or other changes without further notice to this document and any product described herein. Diodes Incorporated does not assume any liability arising out of the application or use of this document or any product described herein; neither does Diodes Incorporated convey any license under its patent or trademark rights, nor the rights of others. Any Customer or user of this document or products described herein in such applications shall assume all risks of such use and will agree to hold Diodes Incorporated and all the companies whose products are represented on Diodes Incorporated website, harmless against all damages.

Diodes Incorporated does not warrant or accept any liability whatsoever in respect of any products purchased through unauthorized sales channel.

Should Customers purchase or use Diodes Incorporated products for any unintended or unauthorized application, Customers shall indemnify and hold Diodes Incorporated and its representatives harmless against all claims, damages, expenses, and attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized application.

Products described herein may be covered by one or more United States, international or foreign patents pending. Product names and markings noted herein may also be covered by one or more United States, international or foreign trademarks.

This document is written in English but may be translated into multiple languages for reference. Only the English version of this document is the final and determinative format released by Diodes Incorporated.

LIFE SUPPORT

Diodes Incorporated products are specifically not authorized for use as critical components in life support devices or systems without the express written approval of the Chief Executive Officer of Diodes Incorporated. As used herein:

- A. Life support devices or systems are devices or systems which:
 - 1. are intended to implant into the body, or
 - 2. support or sustain life and whose failure to perform when properly used in accordance with instructions for use provided in the labeling can be reasonably expected to result in significant injury to the user.
- B. A critical component is any component in a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or to affect its safety or effectiveness.

Customers represent that they have all necessary expertise in the safety and regulatory ramifications of their life support devices or systems, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of Diodes Incorporated products in such safety-critical, life support devices or systems, notwithstanding any devices- or systems-related information or support that may be provided by Diodes Incorporated. Further, Customers must fully indemnify Diodes Incorporated and its representatives against any damages arising out of the use of Diodes Incorporated products in such safety-critical, life support devices or systems.

Copyright © 2016, Diodes Incorporated

www.diodes.com